

Low Power (5mm x 5mm) MMIC

Khaled Elgaid

Iain Thayne

University of Glasgow

kelgaid@elec.gla.ac.uk




Presentation Outline

- **RF TX/TR Systems Options**
- **RF TX/TR Components**
 - **Active (Transistor)**
 - DC – Power Consumption
 - RF
 - Noise
 - **Passive**
 - Capacitors
 - Spiral inductors
 - **Designed Subsystems MMICs**
 - Oscillator
 - Amplifier
- **5x5 RF TX/TR MMIC**
- **Conclusions**



RF System Components

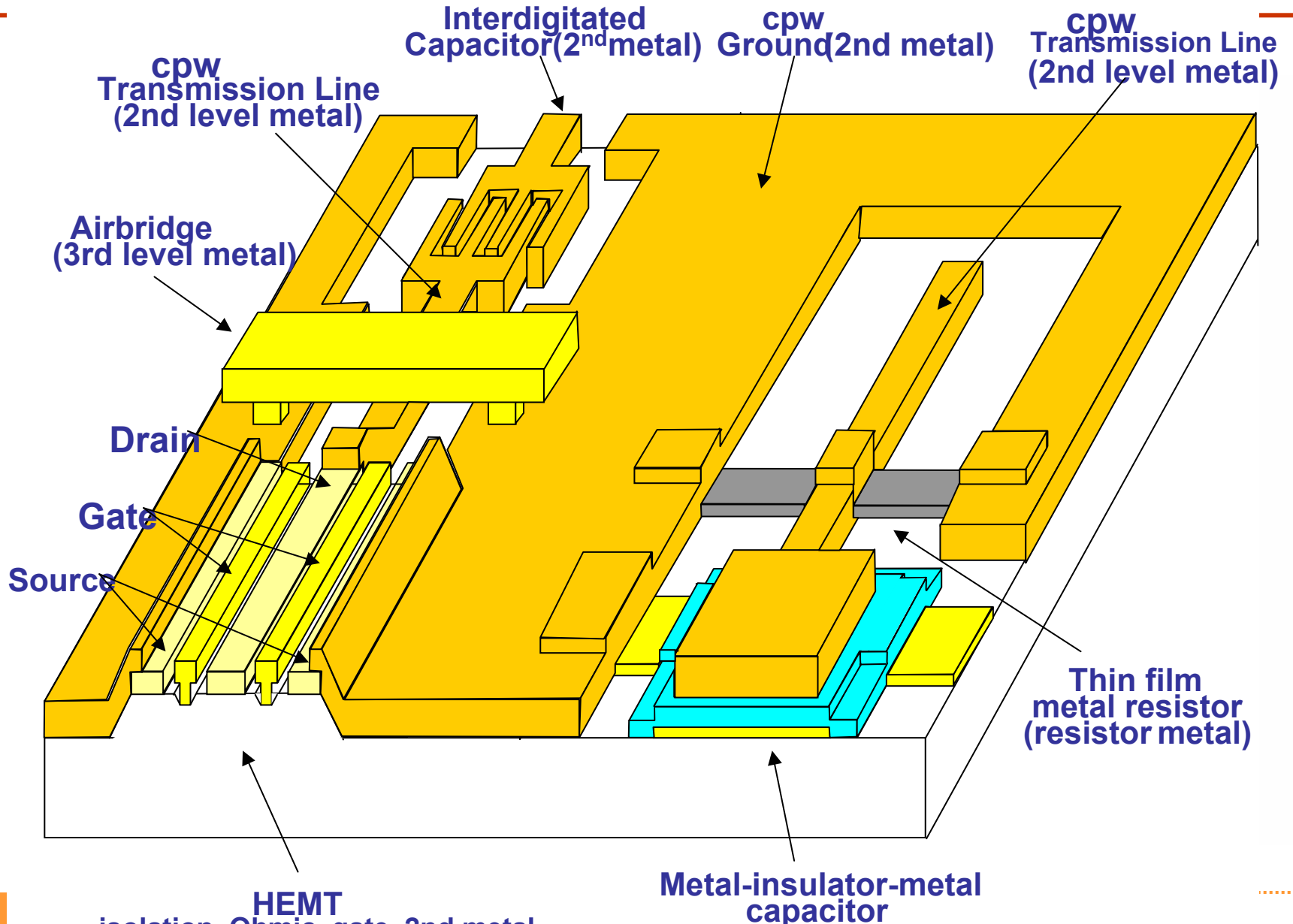

Active (Transistor) DC

Output characteristics

mHEMT

2 x 50 μ m gate width

50nm T-gate

V_{ds} 0V - 1.0 V

V_{gs} = 0V - 1.0 V in - 0.1 V steps


Low power operation mode < 600 μ W

V_{ds} 0.3 to 0.6V

V_{gs} -0.8V

I_{ds} = 0.8mA - 1.15mA

Gate leakage current < 1 μ A

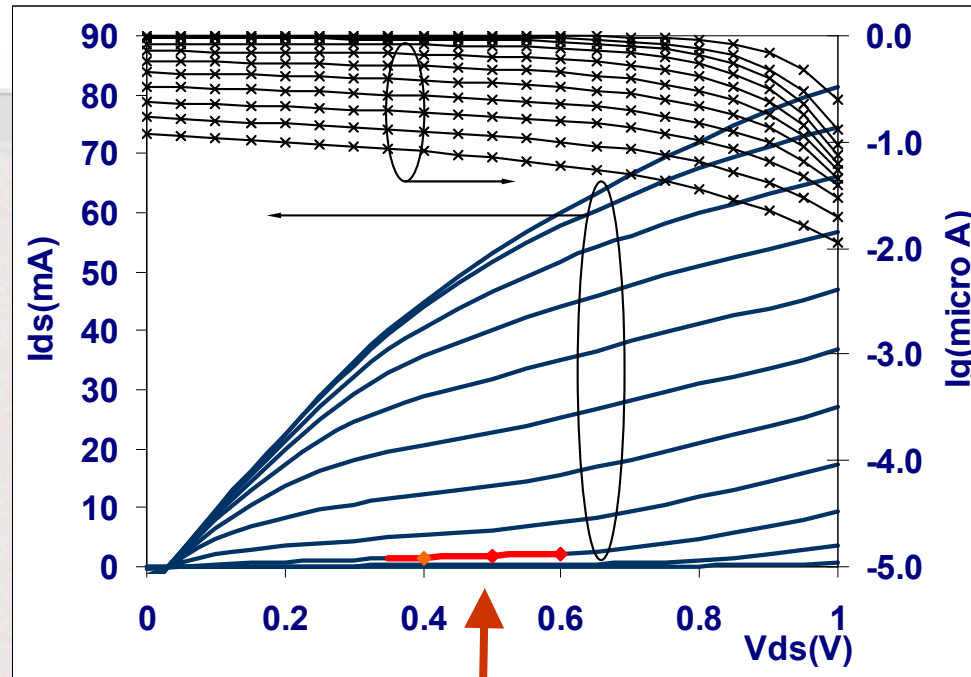

DC power consumption could be reduced further by reducing device physical size

Active (Transistor) DC

Transfer characteristics


mHEMT

2 x 50 μ m gate width

50nm T-gate

V_{ds} 0.3V to 1.0V in 0.1 steps

V_{gs} = 0V to -1.0 V in -0.1 V steps

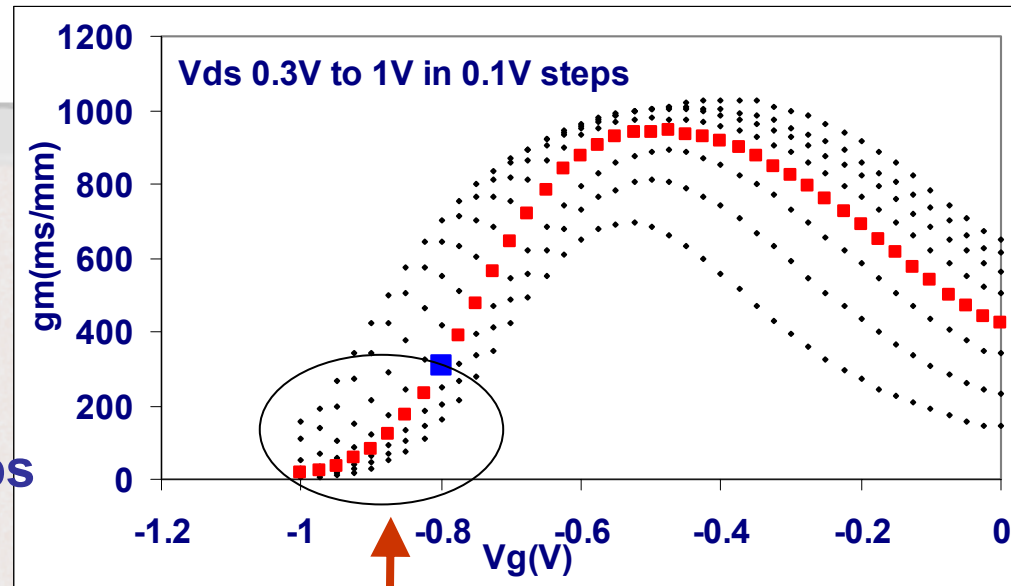

Low power operation mode < 600 μ W

V_{ds} 0.3 to 0.6V

V_{gs} < -0.8V

I_{ds} = 0.8mA – 1.15mA

Transconductance (g_m) ~ 310 ms/mm

Active (Transistor) RF

RF Performance

mHEMT

2 x 50 μ m gate width

50nm T-gate


V_{ds} 0.6 V

V_{gs} = - 0.8 V

The device showed
Exceptionally high RF
performance of

$f_T \sim 60\text{GHz}$

at Low power operation mode < 600 μ W

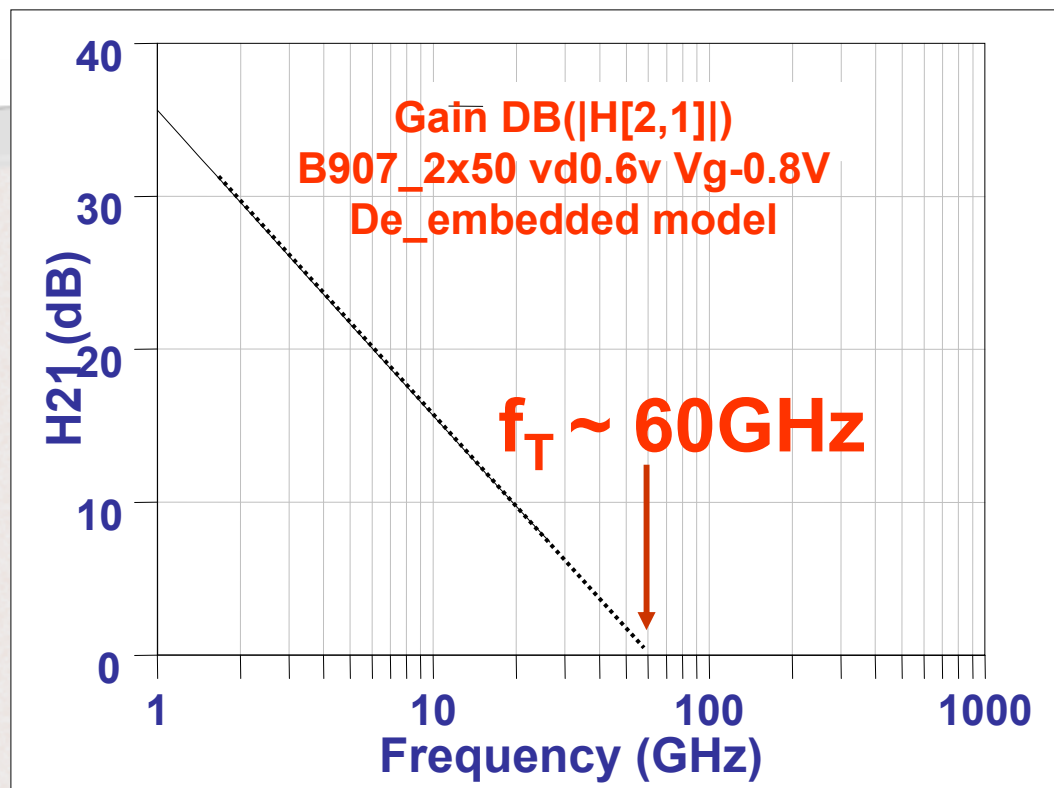

Higher Operating Frequencies ~ 25GHz TX/TR is possible

Active (Transistor) NOISE

Noise Figure

mHEMT

2 x 50 μ m gate width

50nm T-gate


V_{ds} 0.6 V

V_{gs} = - 0.8 V

Low power operation mode ~ 600 μ W

Exceptionally low noise < 1.3 dB up to 26GHz


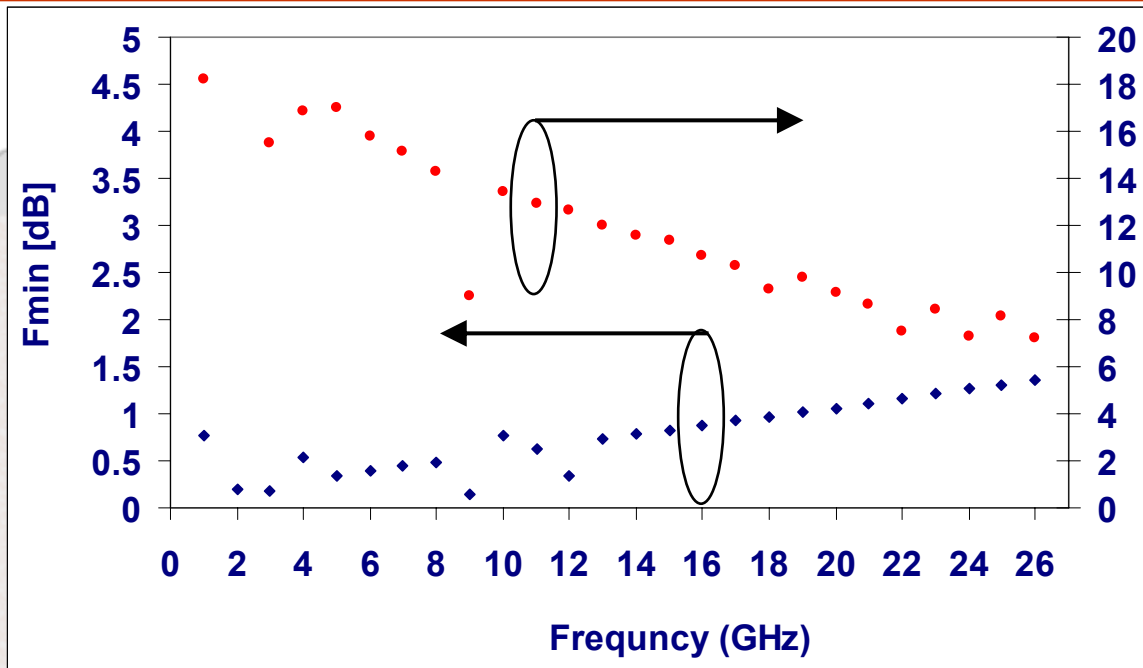
High Associated Gain performance of 7.3dB and better up to 26GHz



Passive Components

Capacitors

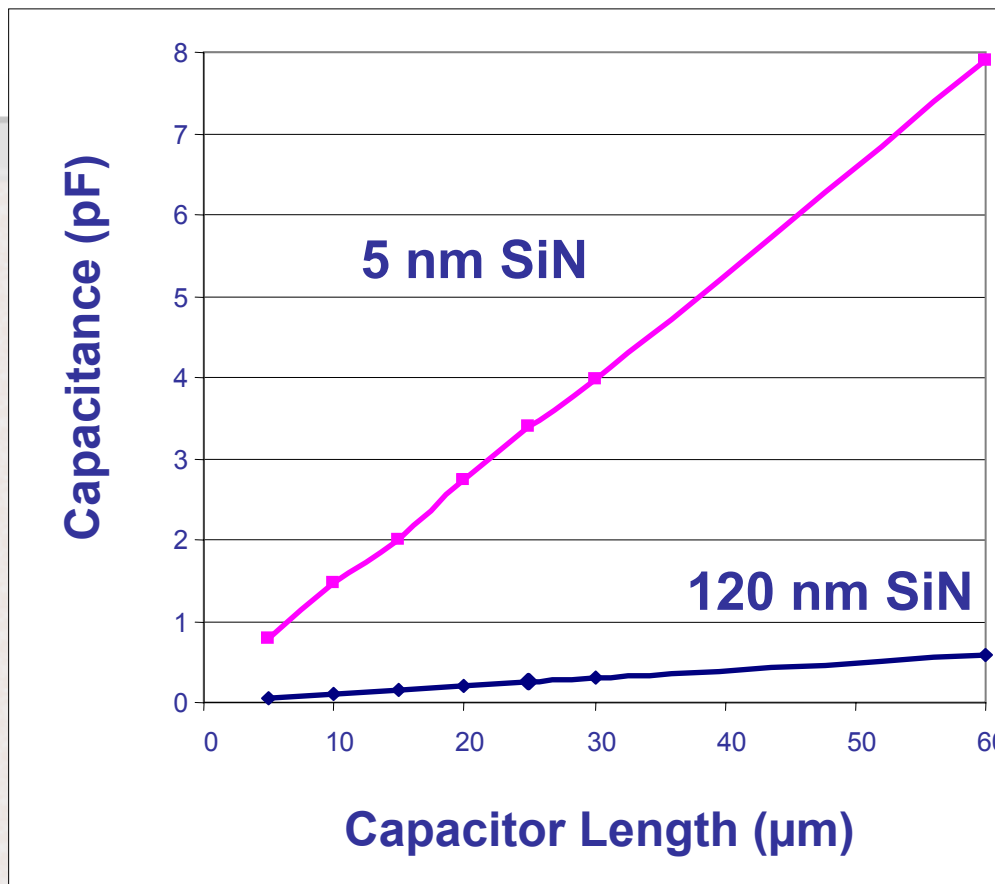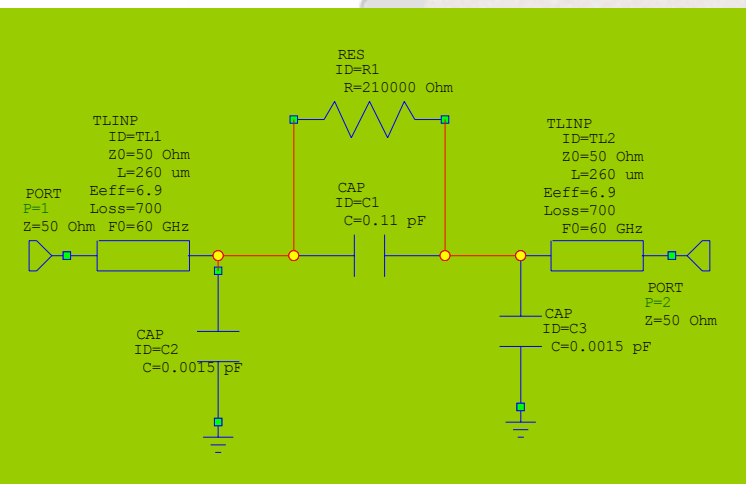20 μm wide MIM
5 – 60 μm Length
SiN Thickness 5nm and 120nm
SiN deposited at 22°C



Capacitance Density = 7 fF/ μm^2

Using Novel 5nm thick SiN MIM capacitors, Capacitance increased by 13 fold

REDUCE CIRCUIT SIZE – LOSS

Passive Components

Inductors



Build a Library model

Investigate Inductor Q

- Spiral
- Square
- different geometry

What are the steps

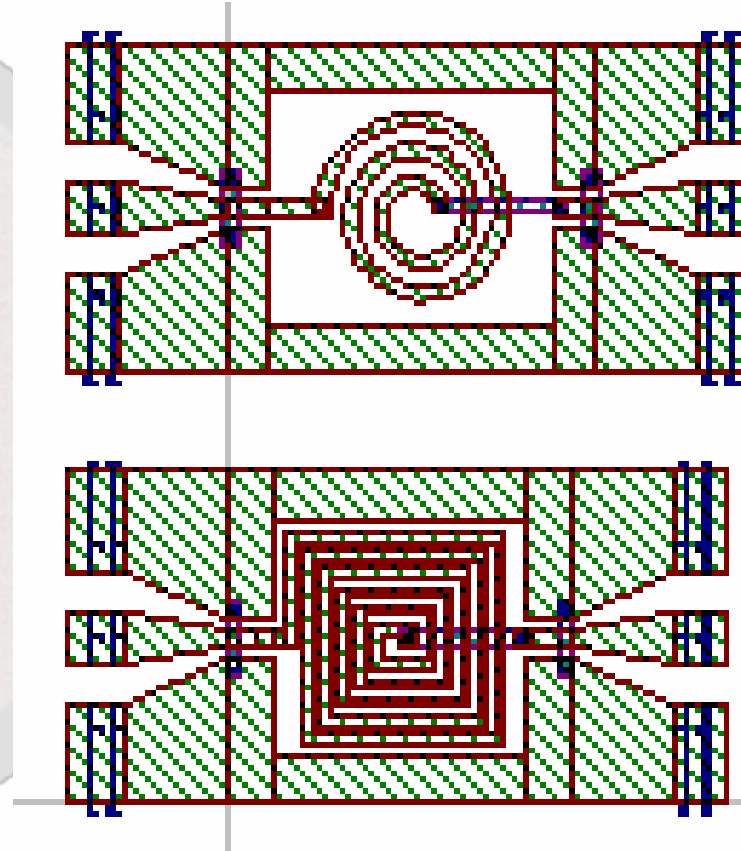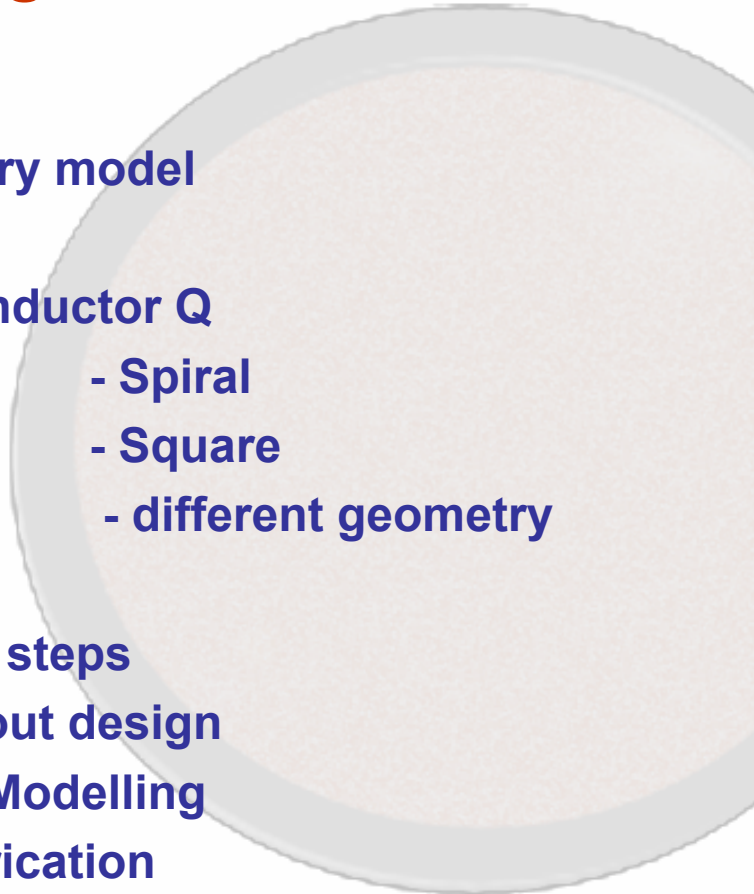- Layout design
- EM Modelling
- Fabrication
- Measurements
- Extract modelling



Designed Subsystems MMICs

2.45 GHz MMIC Oscillator

mHEMT

Gate Length = 50 nm T-gate

Gate width = 2x50 μm



$V_{ds} = 0.6\text{V}$

$V_{gs} = -0.8\text{V}$

$I_d = 1.15\text{mA}$

DC power consumption $\sim 600\mu\text{W}$

Chip size 2.3x1.2mm

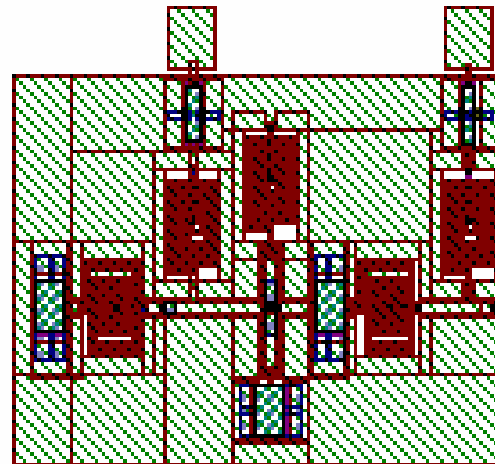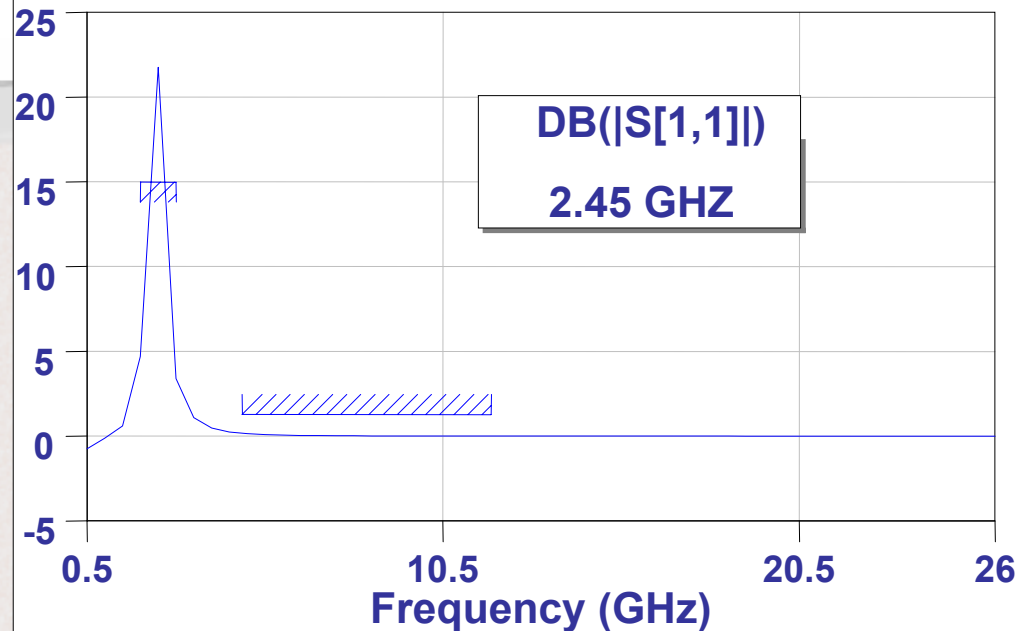

Designed Subsystems MMICs

2.45 GHz MMIC Amplifier

Single Stage

mHEMT

Gate Length = 50 nm T-gate

Gate width = 2x50 μm

$V_{ds} = 0.6\text{V}$

$V_{gs} = -0.8\text{V}$

$I_d = 1.15\text{mA}$



DC power consumption $\sim 600\mu\text{W}$

Gain $\sim 9\text{dB}$

Return Loss $< -8\text{dB}$

Isolation $< -27\text{dB}$

Chip size 1.25x1.2mm

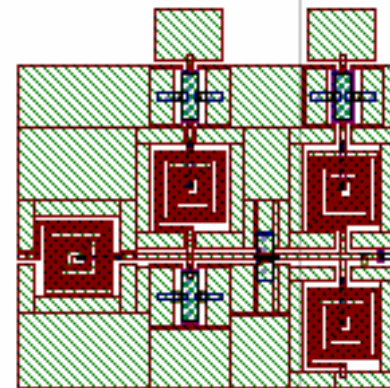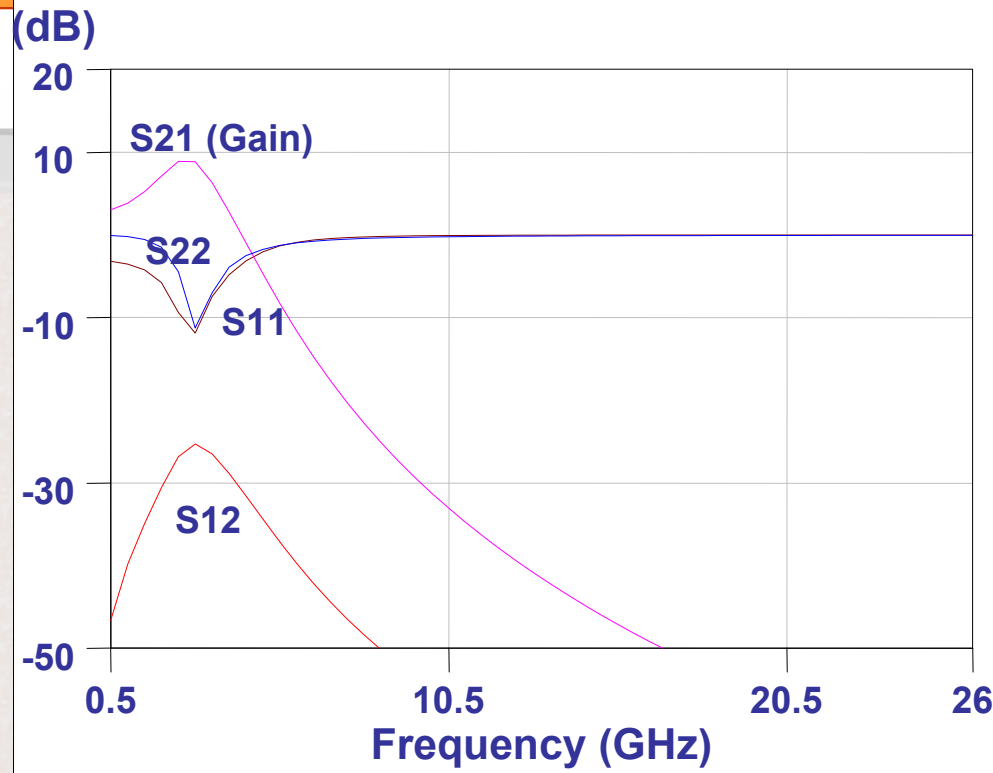

Designed 5mmx5mm TX/TR System MMICs

Layout of 4 Designed TX/TR
in a 5mmx5mm

TOTAL DC Power
consumption for the TX/TR
system ~ 1.2mW

Both TX/TR are **ON**

Chip size ~ 2.5mmx2.5mm

Amplifier


5mm

Detector

To Antenna

FET Switch

Oscillator

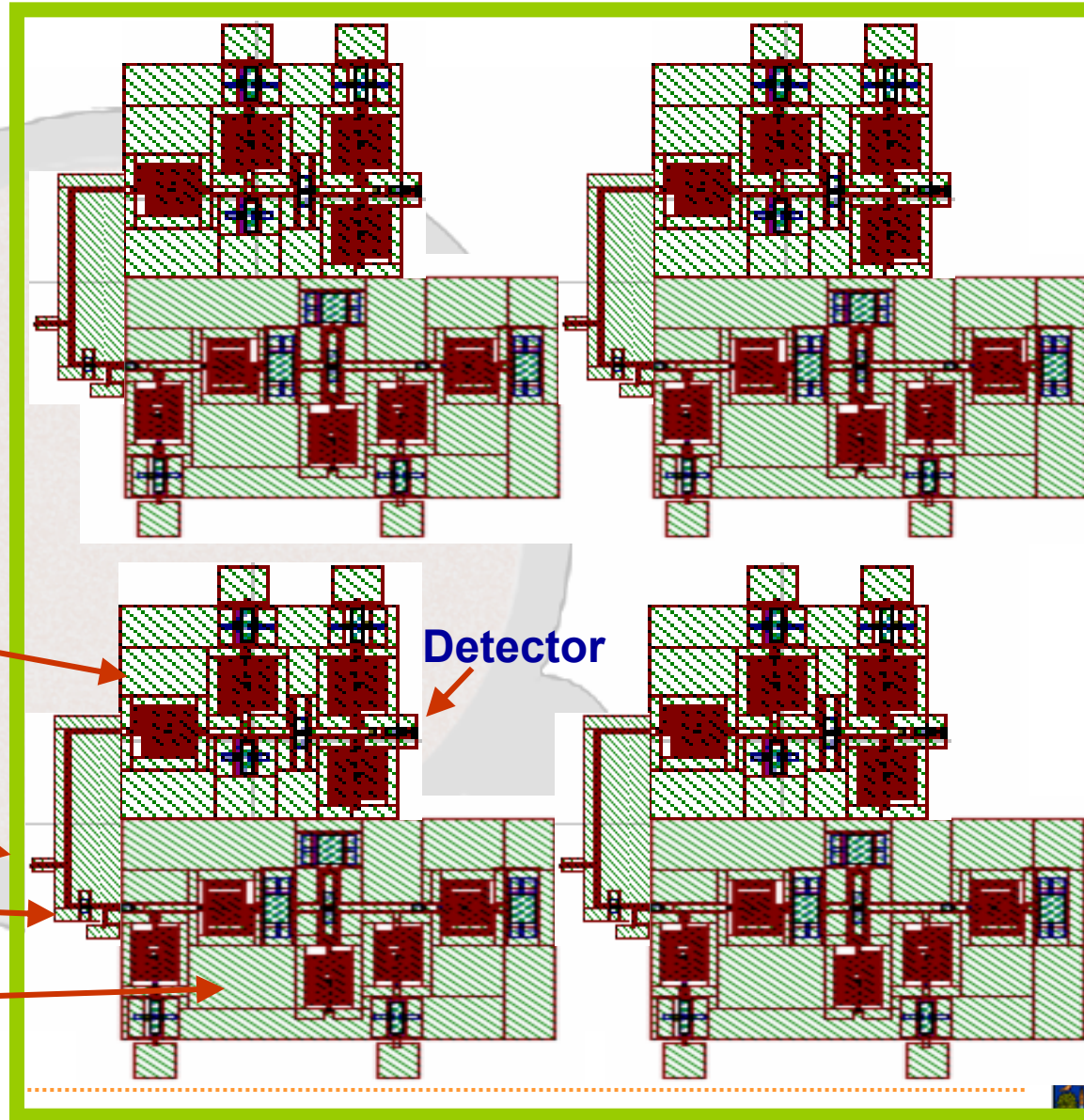

Conclusions

• WE have Investigated three Possible RF TX/TR Systems

• Active devices been Develop

- Very Low DC Power Consumption
- High Gain
- Excellent RF Performance at low power mode ft ~ 60GHz
- Low Noise Figure

• Compact Capacitors using very thin (5nm) SiN Dielectric SiN

• Inductors Equivalent Circuit models is required (for lower frequency operation)

• MMIC subsystems been Designed

- LNA and Oscillator ~DC Power Consumption ~ 600W

• MMIC been Designed

- Chip size ~ 2.5mm x 2.5mm, with low power consumption
- Higher Frequency ~20GHz System should be considered
 - Easier antenna integration
 - Allow different design methodology